# Make a Light up Cube

**SLQ Wiki Fabrication Lab 2025/11/29 00:43** 


# Make a Light up Cube



:facilities:fablab:inductions:handtools:screen shot 2020-11-09 at 10.59.27 am.png
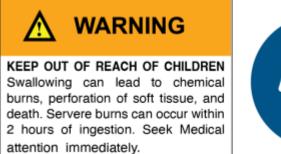
# ANYONE SEEKING TO ADAPT THIS WORKSHOP SHOULD CONSIDER THE FOLLOWING INFORMATION.

WARNING - This workshop makes use of small coin cell/ button batteries.





In December 2020, the Australian Government made mandatory safety and information standards for button/coin batteries and consumer goods that contain button/coin batteries (the standards). The standards included an 18 month transition period and became mandatory from 22 June 2022. From 22 June 2022 manufacturers, importers, wholesalers and retailers of button/coin batteries or consumer goods that contain button/coin batteries supplied to Australia, must comply with the applicable Australian mandatory safety and information standards. Supplying or

selling non-compliant products to consumers in Australia is illegal. The four mandatory standards are as follows:

- Consumer Goods (Products Containing Button/Coin Batteries) Safety Standard
- Consumer Goods (Products Containing Button/Coin Batteries) Information Standard
- Consumer Goods (Button/Coin Batteries) Safety Standard
- Consumer Goods (Button/Coin Batteries) Information Standard

## **Summary**

Lightup Box is a short - 10-15 minute - community engagement activity designed to accompany basic explanation of electronics like the Electronics 101.

#### **Materials**

These materials are per participant if not specified otherwise.

- 1. 1 x CR2032 Battery (See warning above)
- 2. 4 x LED (in one colour)
- 3. 3d printed box (see below)
- 4. Mini breadboard.
- 5. 2x resistor (75 Ohms)
- 6. jumper wires

#### **Tools**

Multimeter Hot Glue gun


#### Instructions


#### **Step Zero: Prep**

cut off **B** end of usb cable and terminate positive (red) and ground (black) conductors with a male jumper cable lead as pictured below. (secure other conductors against short circuits with heat shrink). one for each participant.
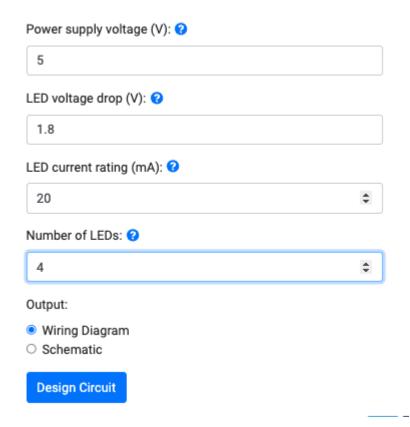
## **Step One:**

Use LED Calculator to get a circuit diagram



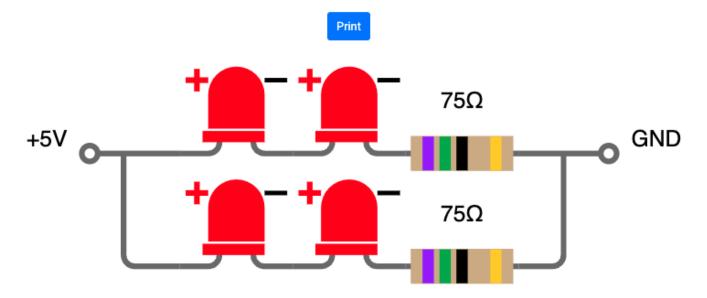


- · You will need 2 x 75 ohm 1/8 watt resistors.
- The 75 ohm resistor is color coded: Violet, Green, Black, Gold.
  - · Each 75 ohm resistor consumes 30 milliwatt.
  - · Total power consumed by the resistors is 60 milliwatt.
  - · Total power consumed by the LEDs is 144 milliwatt.
  - · Total power consumed by the circuit is 204 milliwatt.
  - · Total current drawn by the circuit is 40 milliampere.
- The resistor values are calculated based on the common ±5% tolerance resistors.
  - · Make sure to wire the LEDs in the correct direction as shown below.
  - · Always leave some space for the resistors to breathe. They might get hot.



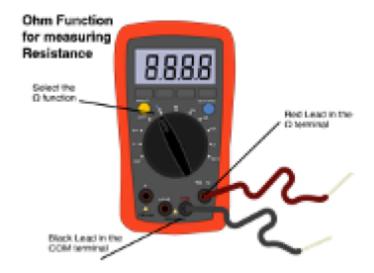
#### **Step Two:**

Review how a multimeter and breadboard works. Familiarise /Test LEDs with CR2032 Battery use the multimeter on the Continuity setting to demo how the bread boards work



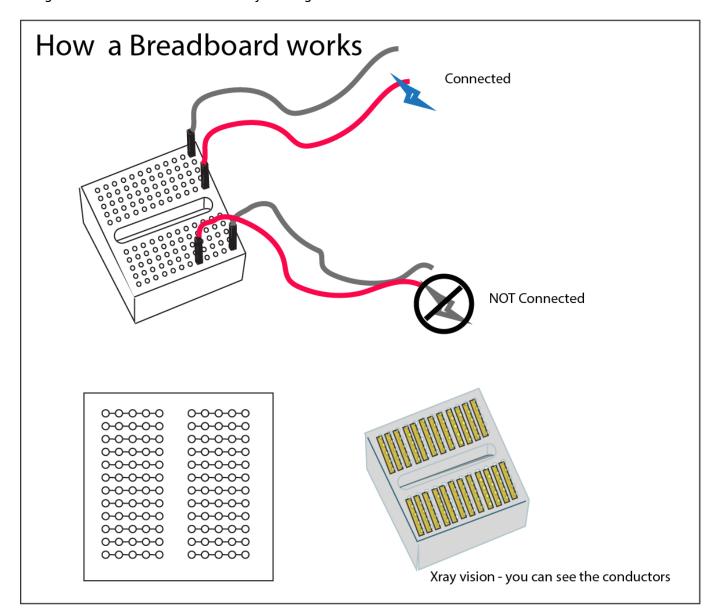
Select the continuety setting by • selecting Ohm on the Dial  $\Omega$  • And use the blue button in the image above to select the continuity setting  $\delta$ 



## **Step Three:**

Work out how you are going to use the bread board to connect your circuit.

Here's how i did it

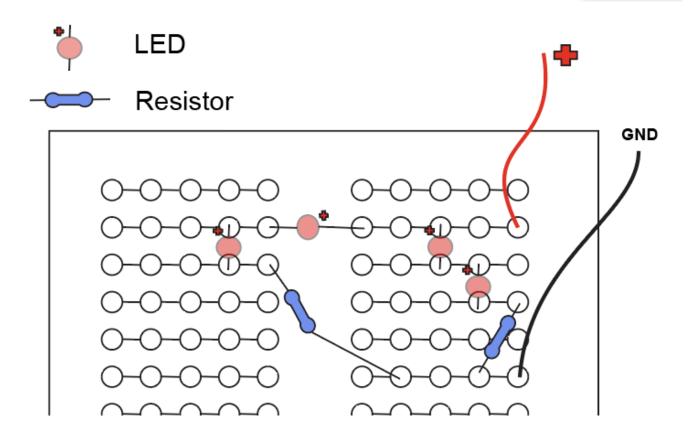

## **Step Four:**

Assemble you circuit on you bread board and test it with the power source.

#### **Step Five:**

if it works hot glue you're components in place and install the circuit into you 3d printed box Extension Activity

## **Activity Extensions**

Work out how you could use lithophanemaker to add an image to the 3D printed box

#### **Files**

lightbox.stl

# **Acknowledgement**

We acknowledge Aboriginal and Torres Strait Islander peoples and their continuing connection to land and as custodians of stories for millennia. We respectfully acknowledge the land on which we all meet today, and pay our respects to elders past, present and emerging.